

# UART Implementation on FPGA with System Verilog

Nilakna D. Warushavithana

May 23, 2025

# Contents

<b>1</b>	<b>UART: Introduction</b>	<b>4</b>
<b>2</b>	<b>Transmitter</b>	<b>5</b>
2.1	Introduction . . . . .	5
2.2	RTL Code in System Verilog . . . . .	6
2.3	State Machine: Transmitter . . . . .	7
2.4	RTL design view . . . . .	7
2.5	Verification Test Bench in System Verilog . . . . .	8
2.6	Test bench simulation for Verification . . . . .	9
<b>3</b>	<b>Receiver</b>	<b>10</b>
3.1	Introduction . . . . .	10
3.2	RTL Code in System Verilog . . . . .	11
3.3	State Machine: Receiver . . . . .	12
3.4	RTL design view . . . . .	12
3.5	Verification Test Bench in System Verilog . . . . .	13
3.6	Test bench simulation . . . . .	14
<b>4</b>	<b>Bidirectional UART Transceiver</b>	<b>15</b>
4.1	Introduction . . . . .	15
4.2	RTL Code in System Verilog . . . . .	16
4.3	RTL design view . . . . .	16
4.4	Verification Test Bench in System Verilog . . . . .	17
4.5	Test bench simulation . . . . .	18
<b>5</b>	<b>Implementation on DEO Nano FPGA</b>	<b>20</b>
5.1	Introduction . . . . .	20
5.2	Pin plan . . . . .	21
5.3	RTL Code of the top module . . . . .	22
5.4	RTL design view . . . . .	22
5.5	Results on FPGA . . . . .	23

## List of Figures

1	RTL design of transmitter module . . . . .	6
2	Transmitter state machine . . . . .	7
3	Transmitter module RTL . . . . .	7
4	Test bench code of transmitter module . . . . .	8
5	Transmitter test bench simulation waveforms for verification . . . . .	9
6	RTL design of receiver module . . . . .	11
7	Receiver state machine . . . . .	12
8	Receiver module RTL . . . . .	12
9	Test bench code of receiver module . . . . .	13
10	Receiver test bench simulation waveforms for verification . . . . .	14
11	RTL design of UART transceiver module . . . . .	16
12	UART transceiver module block diagram . . . . .	16
13	Test bench code of UART transceiver module . . . . .	17
14	UART test bench simulation timing diagram waveforms . . . . .	18
15	Vivado Simulation . . . . .	19
16	Pin planner for DEO Nano Board . . . . .	21
17	Top module RTL code for FPGA . . . . .	22
18	UART top module block diagram . . . . .	22
19	Sample data sending from UART TX to RX . . . . .	23
20	RX is '1 when transmitter sends no data . . . . .	24

# 1 UART: Introduction

The Universal Asynchronous Receiver-Transmitter (UART) represents one of the most fundamental and widely adopted serial communication protocols. This implementation demonstrates a complete UART communication system designed for FPGA deployment. The UART protocol is simple, reliable, and has minimal hardware requirements, making it suitable for many applications.

The UART protocol operates as an asynchronous serial communication standard; so, it does not need a shared clock signal between communicating devices. Data transmission occurs through a predetermined frame structure consisting of a start bit, data payload, optional parity bit, and stop bit(s). Since the clock is not shared, a timing agreement between the transmitter and receiver should be there. It is typically achieved through standardized baud rates such as 9600, 38400, 115200, or higher frequencies, depending on the requirements.

Protocol specifications for this implementation follow the standard 8N1 configuration: eight data bits, no parity bit, and one stop bit. Each transmitted frame begins with a start bit (logic low) that signals the beginning of data transmission, followed by eight data bits starting from the LSB, and concludes with a stop bit (logic high) that returns the communication line to its idle state. The idle condition maintains the transmission line at logic high, providing a clear reference for start bit detection.

This FPGA implementation utilizes a hierarchical design methodology, separating transmission and reception functionality into separate modules while maintaining protocol through parameter management and signal coordination. The design uses 50 MHz system clock on the DEO-Nano board with 115200 baud operation (434 clock cycles per bit period). The implementation incorporates digital design practices, including parameterized modules, state machine design, and robust reset handling to ensure reliable operation in practical deployment scenarios.

## 2 Transmitter

### 2.1 Introduction

The transmitter module implements the UART transmission using a finite state machine (FSM) with two primary states: `IDLE` and `SEND`. The module accepts parallel data input and serializes it for transmission according to the UART protocol standard. Upon receiving a valid send signal (`send_valid`), the transmitter creates the complete UART frame by adding a start bit (logic 0), the payload (8-bit data), and a stop bit (logic 1) into a 10-bit packet stored in `send_packet`.

The transmission happens through precise timing control using two counters: `clk_cnt` for pulse width timing and `data_cnt` for counting data bits to track bit position. The pulse width counter ensures each transmitted bit maintains the correct duration based on the configured baud rate (`PULSE_WIDTH` parameter). During transmission, the module right shifts the data packet, outputting each bit sequentially through the tx output line. The transmitter keeps the tx line at logic high during idle periods, maintaining standard UART specifications.

Finite state machine and the state transmissions ensure reliable communication. The module maintains `tx_ready` only during the `IDLE` state, preventing data corruption from early transmission requests. Clock considerations are managed by synchronous reset implementation, ensuring predictable behavior during system initialization. Our parameterized design allows for flexible configuration of word size, pulse width, and packet size, making it adaptable to various communication requirements while maintaining protocol requirements.

## 2.2 RTL Code in System Verilog

```

`timescale 1ns / 1ps

module transmitter #(
    parameter
        WORD_SIZE = 8,          // 8 bits per word
        PULSE_WIDTH = 4,        // PULSE_WIDTH = CLOCK_FREQ/BAUD, CLOCK_FREQ = 100000000, BAUD = 115200, CLK_PERIOD = 10
        PACKET_SIZE = 10        // start, word, stop
)
(
    input logic clk, rstn, send_valid,
    input logic [WORD_SIZE-1:0] data_bits,
    output logic tx_ready, tx
);

typedef enum logic [1:0] {IDLE, SEND} statetype;
statetype state;

localparam PACKET_WIDTH_BITS = $clog2(PACKET_SIZE);
localparam PULSE_WIDTH_BITS = $clog2(PULSE_WIDTH);

// initialize data packet to transmit
logic [PACKET_SIZE-1:0] data_packet;
logic [PACKET_SIZE-1:0] send_packet;

// assign start bit and stop bit to data packet
assign send_packet = {1'b1, data_bits, 1'b0}; // stop bit = 1, data, start bit = 0

// initiate a tx register to update the bit to send
logic tx_reg;

// assign output bit
assign tx = tx_reg;

// counters for packet length in pulses and pulse length in clocks
logic [PACKET_WIDTH_BITS-1:0] data_cnt;
logic [PULSE_WIDTH_BITS-1:0] clk_cnt;

// transmitter is ready to transmit in IDLE state
assign tx_ready = (state==IDLE);

// state machine
always_ff @(posedge clk or negedge rstn) begin
    if (!rstn) begin
        state <= IDLE;
        data_packet <= '1;
        data_cnt <= 0;
        clk_cnt <= 0;
        tx_reg <= 1'b1; // UART line is high when idle
    end
    else case (state)
        IDLE: if (send_valid) begin
            state <= SEND;
            data_packet <= send_packet;
            data_cnt <= 0;
            tx_reg <= send_packet[0];
        end
        SEND: begin
            if (clk_cnt == PULSE_WIDTH-1) begin
                clk_cnt <= 0; // reset the clock count
                if (data_cnt == PACKET_SIZE-1) begin
                    data_packet <= '1;
                    data_cnt <= 0;
                    state <= IDLE;
                    tx_reg <= 1'b1; // Set line high when returning to idle
                end
                else begin
                    data_cnt <= data_cnt + 1;
                    data_packet <= (data_packet >> 1);
                    tx_reg <= data_packet[1];
                end
            end
            else clk_cnt <= clk_cnt + 1; // if pulse is not complete count the clocks
        end
    endcase
end
endmodule

```

Figure 1: RTL design of transmitter module

## 2.3 State Machine: Transmitter

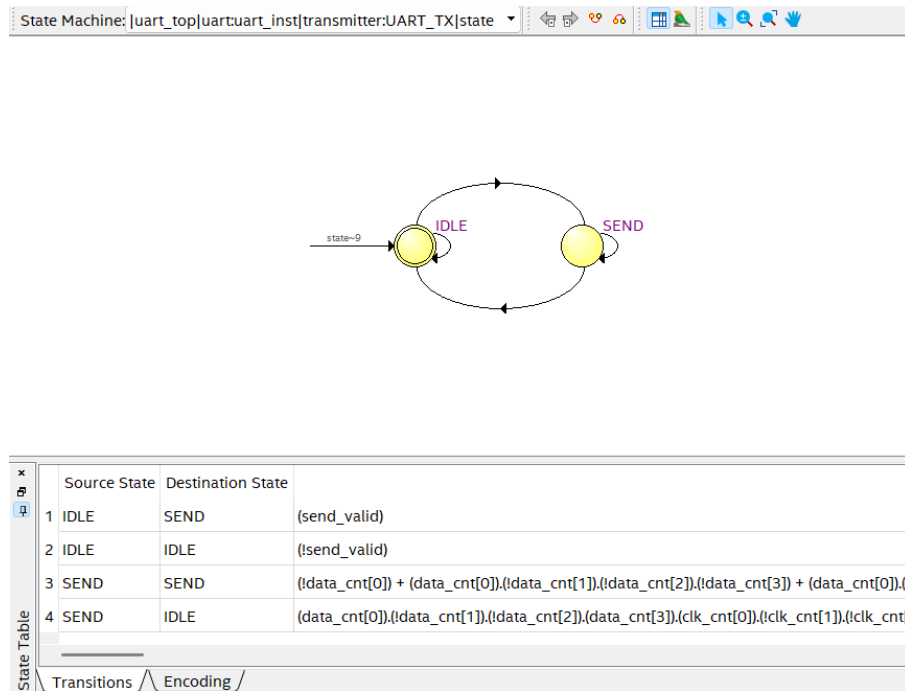


Figure 2: Transmitter state machine

## 2.4 RTL design view

 


Figure 3: Transmitter module RTL

## 2.5 Verification Test Bench in System Verilog

```

`timescale 1ns / 1ps
module transmitter_tb;
// timeunit 1ns; timeprecision 1ps;

// parameters
localparam WORD_SIZE = 8, // 8 bits per word
            PULSE_WIDTH = 4, // PULSE_WIDTH = CLOCK_FREQ/BAUD, CLOCK_FREQ = 100000000, BAUD = 115200, CLK_PERIOD = 10
            PACKET_SIZE = 10, // start, word, stop
            CLK_PERIOD = 10; // 100MHz

// signals in test bench
logic clk = 0;
logic rstn = 0; // start in reset mode
logic send_valid = 0;
logic tx_ready;
logic tx;
logic [WORD_SIZE-1:0] data_bits; // data to/before transmit
logic [WORD_SIZE-1:0] test_values [0:9]; // words for 10 test cases

// instantiate the transmitter
transmitter #(
    .WORD_SIZE(WORD_SIZE),
    .PULSE_WIDTH(PULSE_WIDTH),
    .PACKET_SIZE(PACKET_SIZE))
dut (
    .clk(clk),
    .rstn(rstn),
    .send_valid(send_valid),
    .data_bits(data_bits),
    .tx_ready(tx_ready),
    .tx(tx)
);

// clock generation
always # (CLK_PERIOD/2) clk <= !clk; // 5 = CLK_PERIOD/2

// generate test cases
initial begin
    test_values[0] = 8'h55;
    test_values[1] = 8'hA3;
    test_values[2] = 8'h7E;
    test_values[3] = 8'h00;
    test_values[4] = 8'hFF;
    test_values[5] = 8'hC3;
    test_values[6] = 8'h3C;
    test_values[7] = 8'h5A;
    test_values[8] = 8'h81;
    test_values[9] = 8'h1E;
end

// test sequence
initial begin
    $dumpfile ("dump.vcd"); $dumpvars;

    // reset
    #20 rstn = 1; // remove reset after 20 ns (2 clks)
    repeat(5) @(posedge clk) #1;

    // send test cases (10 words)
    for (int i = 0; i < 10; i = i+1) begin
        // generate random 10 test cases (10 words)
        // repeat (10) begin
            //repeat ($urandom_range(1,20)) @(posedge clk);
            repeat(10) @(posedge clk);

            wait (tx_ready == 1); // wait till tx is ready. ready in IDLE

            // data_bits = $urandom(); // test pattern [7:0] recieve is 0,01001001,1
            data_bits = test_values[i];

            @(posedge clk) #1 send_valid = 1; // start sending
            @(posedge clk) #1 send_valid = 0; // send signal pulse ends

            #10 $display("sending 0,%b,1", data_bits);
        end
    end


    // count uart bits - for waveform
    int bits;
    initial forever begin
        bits = 0;
        wait (!tx);
        for (int j = 0; j < PACKET_SIZE; j = j+1) begin
            bits += 1;
            repeat (PULSE_WIDTH) @(posedge clk);
        end
    end
endmodule

```


Figure 4: Test bench code of transmitter module


 
## 2.6 Test bench simulation for Verification



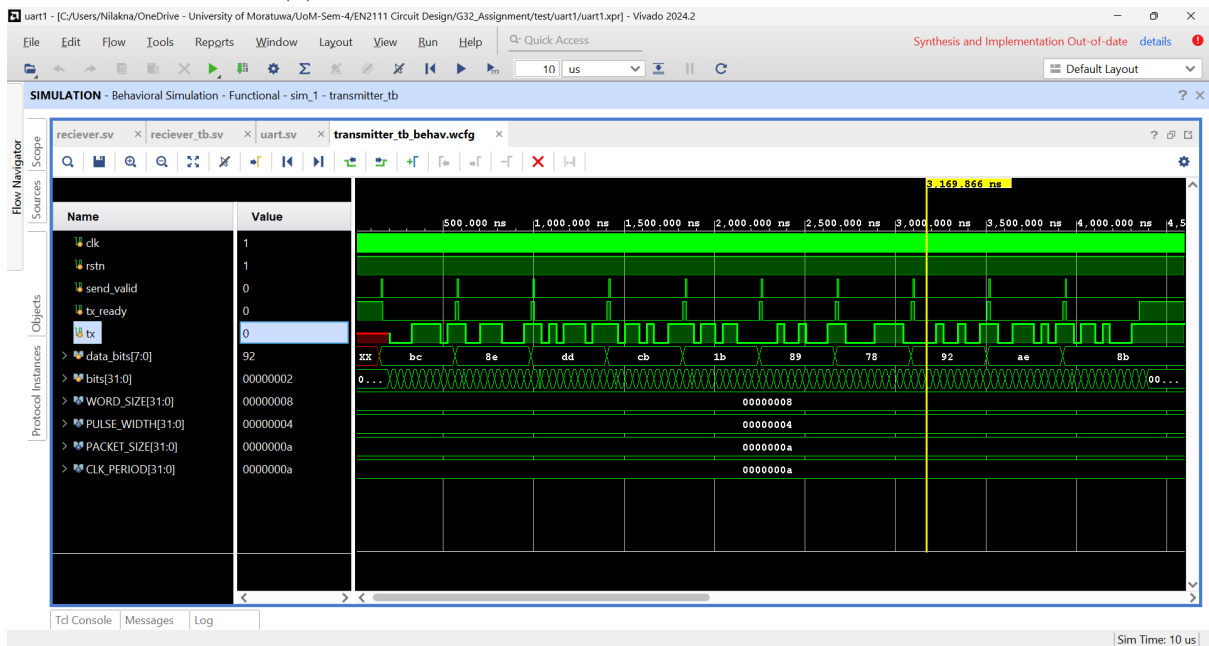(a) Simulation in Quartus Prime - Modelsim Altera



(b) Simulation in Vivado

Figure 5: Transmitter test bench simulation waveforms for verification

## 3 Receiver

### 3.1 Introduction

The receiver module implements an FSM with 4 states: IDLE, START, DATA, and STOP, to decode the incoming UART serial data stream. The design implements timing recovery and bit sampling to ensure reliable data reception even with clock differences between transmitter and receiver systems. The module continuously monitors the rx input line for the start bit transition from idle high to active low.

Upon detecting a start bit, the receiver transitions to the START state and initiates sampling at the middle of the bit by counting to half the pulse width period. Then it transitions to the DATA state, where it sequentially captures 8 data bits and storing them in the `data_bits` register with indexing to maintain bit order. Each bit is sampled after a full pulse width duration to ensure synchronization with the transmitter's timing.

The receiver's timing implementation has 2 counters: `clk_cnt` for bit duration timing and `data_cnt` for tracking received data bits within each word. Error handling is done through state timeout and reset procedures. The module validates frame structure with the stop bit in the STOP state before returning to IDLE. The `rx_valid` signal indicates successful frame reception and data availability, enabling us to process received data. Parameterization supports various word sizes and baud rates while maintaining protocol integrity.

## 3.2 RTL Code in System Verilog

```

timescale 1ns / 1ps
module reciever #(
    parameter WORD_SIZE = 8, // 8 bits per word
                PULSE_WIDTH = 4, // PULSE_WIDTH = CLOCK_FREQ/BAUD, CLOCK_FREQ = 100000000, BAUD = 115200, CLK_PERIOD = 10
                PACKET_SIZE = 10 // start, word, stop
)(
    input logic clk, rstn, rx,
    output logic rx_valid,
    output logic [WORD_SIZE-1:0] data_bits
);

typedef enum logic [1:0] {IDLE, START, DATA, STOP} statetype; // define state data type
statetype state; // create state variable

localparam PULSE_WIDTH_BITS = $clog2(PULSE_WIDTH); // for clock count
localparam WORD_SIZE_BITS = $clog2(WORD_SIZE); // for bit count in word

// counters for pulse and word
logic [PULSE_WIDTH_BITS-1:0] clk_cnt;
logic [WORD_SIZE_BITS-1:0] data_cnt;

// reciever is ready to recieve in IDLE state
assign rx_valid = (state==IDLE);

// state machine
always_ff @(posedge clk or negedge rstn) begin
    if (!rstn) begin
        state <= IDLE;
        data_bits <= '0;
        data_cnt <= 0;
        clk_cnt <= 0;
    end

    else case (state)
        IDLE: begin
            if (rx==0) state <= START; // when we get start bit, go to start state
            end

        START: begin
            if (clk_cnt == PULSE_WIDTH/2-1) begin
                clk_cnt <= 0; // reset clock for data
                data_cnt <= 0; // reset data count
                data_bits <= '0; // reset data_bits register
                state <= DATA; // halfway through start bit, switch to data state
            end
            else clk_cnt += 1; // if not increase clock count
            end

        DATA: begin
            if (clk_cnt == PULSE_WIDTH-1) begin
                clk_cnt <= 0; // reset the pulse count clock
                data_bits[data_cnt] <= rx; // append the recieved bit rx
            end
            if (data_cnt == WORD_SIZE-1) begin
                data_cnt <= 0; // reset data bit count for word
                state <= STOP; // go to STOP state
            end
            else data_cnt += 1; // if word isnt finised, sount data bits
            end
            else clk_cnt += 1; // if not increase pulse clock count
            end

        STOP: begin
            if (clk_cnt == PULSE_WIDTH-1) begin
                state <= IDLE; // go to IDLE state after this
                clk_cnt <= 0; // reset pulse clock
            end
            else clk_cnt += 1; // if not increase pulse clock count
            end
    endcase
end
endmodule

```

Figure 6: RTL design of receiver module

### 3.3 State Machine: Receiver

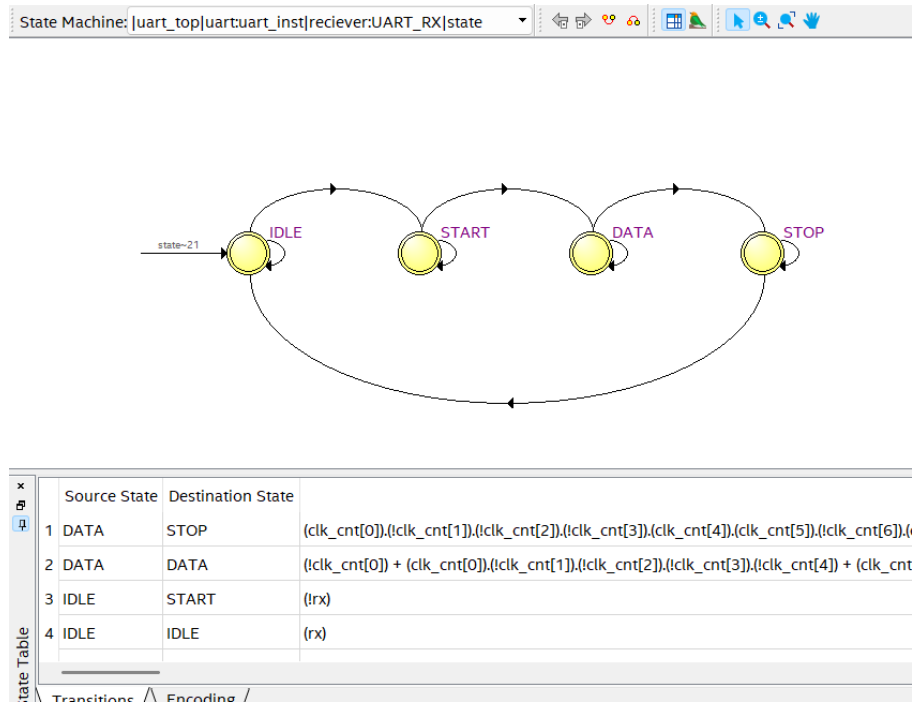


Figure 7: Receiver state machine

### 3.4 RTL design view

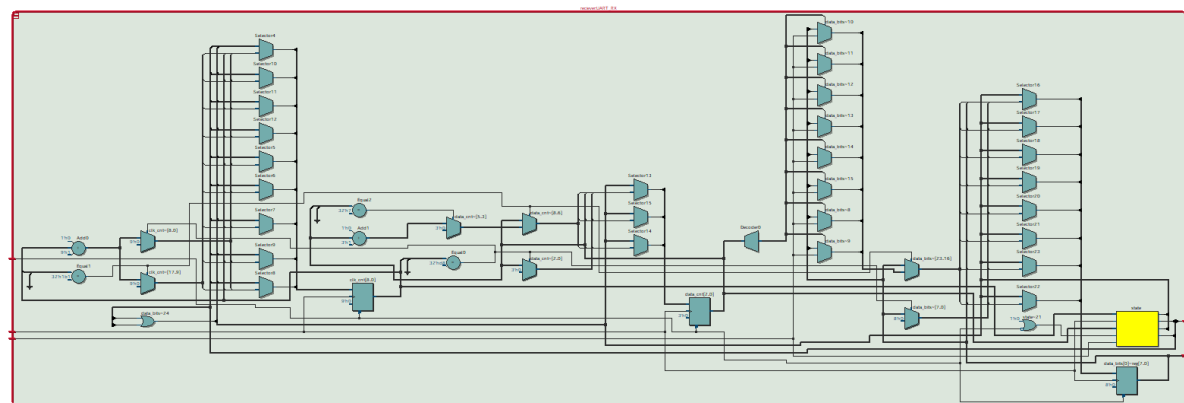


Figure 8: Receiver module RTL

### 3.5 Verification Test Bench in System Verilog

```

`timescale 1ns / 1ps
module reciever_tb;
    //parameters
    localparam WORD_SIZE = 8, // 8 bits per word
               PULSE_WIDTH = 4, // PULSE_WIDTH = CLOCK_FREQ/BAUD, CLOCK_FREQ = 100000000, BAUD = 115200, CLK_PERIOD = 10
               PACKET_SIZE = 10, // start, word, stop
               CLK_PERIOD = 10; // 100MHz

    // signals
    logic clk = 0,
          rstn = 0, // start in reset
          rx = 1,
          rx_valid;
    logic [WORD_SIZE-1:0] data_bits;

    // test bench data and packet simul
    logic [WORD_SIZE-1:0] sample_data;
    logic [WORD_SIZE-1+2:0] sample_packet;
    logic [WORD_SIZE-1:0] test_values [0:9]; // words for 10 test cases

    // instantiate the reciever
    reciever #(
        .WORD_SIZE(WORD_SIZE),
        .PULSE_WIDTH(PULSE_WIDTH),
        .PACKET_SIZE(PACKET_SIZE))
        dut (
            .clk(clk),
            .rstn(rstn),
            .data_bits(data_bits),
            .rx(rx),
            .rx_valid(rx_valid)
        );

    // clock generation
    always #((CLK_PERIOD/2) clk <= !clk; // 5 = CLK_PERIOD/2

    // generate test cases
    initial begin
        test_values[0] = 8'h55;
        test_values[1] = 8'hA3;
        test_values[2] = 8'h7E;
        test_values[3] = 8'h00;
        test_values[4] = 8'hFF;
        test_values[5] = 8'hC3;
        test_values[6] = 8'h3C;
        test_values[7] = 8'h5A;
        test_values[8] = 8'h81;
        test_values[9] = 8'h1E;
    end

    // test sequence
    initial begin
        $dumpfile ("dump.vcd"); $dumpvars;

        // reset
        #20 rstn = 1; // remove reset after 20 ns (2 clks)
        repeat(5) @(posedge clk) #1;

        // send test cases (10 words)
        for (int i = 0; i < 10; i = i+1) begin
            // generate random 10 test cases (10 words)
            // repeat (10) begin
            // generate sample data stream
            // sample_data = $urandom(); // test pattern [7:0] recieve is 0,01001001,1
            sample_data = test_values[i];
            sample_packet = {1'b1, sample_data, 1'b0}; // packet format

            // send these to the reciever
            repeat ($urandom_range(1,20)) @(posedge clk);
            for (int i = 0; i < WORD_SIZE+2; i = i+1)
                repeat (PULSE_WIDTH) @(posedge clk) #1 rx <= sample_packet[i]; // latch bit from the packet

            // for debugging
            #10 $display("Should recieve %b", sample_data);


            // add some delay
            repeat ($urandom_range(1,50)) @(posedge clk);
        end

        // count uart bits - for waveform
        int bits;
        initial forever begin
            bits = 0;
            wait (!rx);
            for (int j = 0; j < PACKET_SIZE; j = j+1) begin
                bits += 1;
                repeat (PULSE_WIDTH) @(posedge clk);
            end
        end
    end
endmodule


```

Figure 9: Test bench code of receiver module

### 3.6 Test bench simulation

 

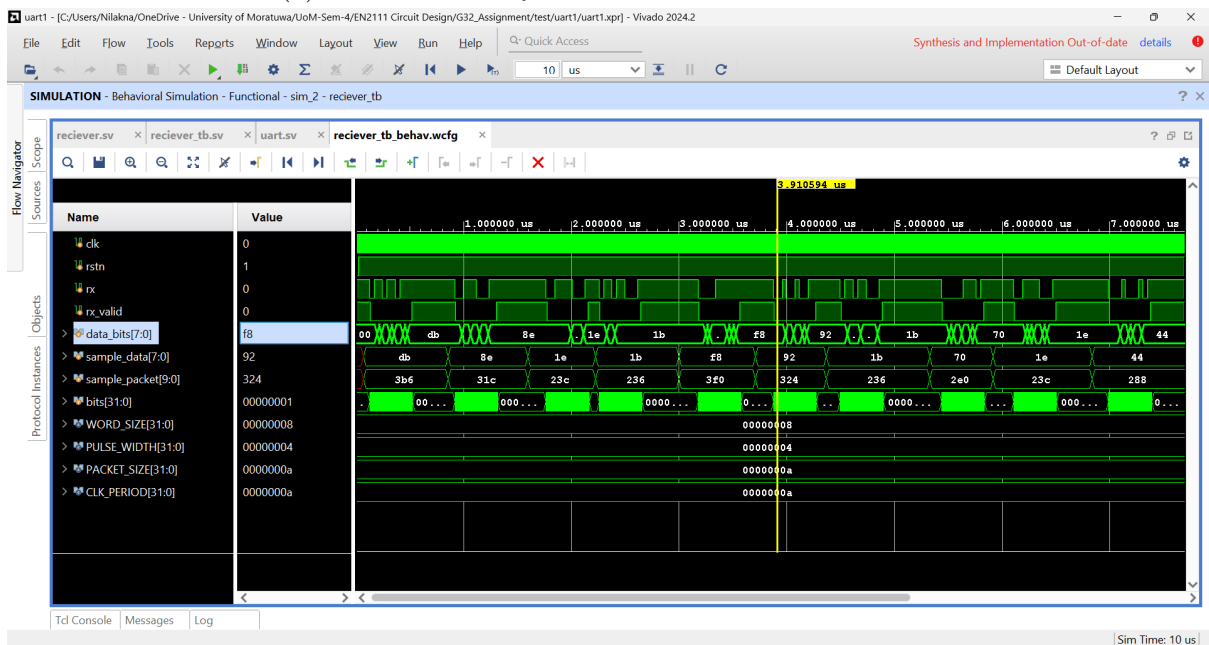(a) Simulation in Quartus Prime - Modelsim Altera



(b) Simulation in Vivado

Figure 10: Receiver test bench simulation waveforms for verification

## 4 Bidirectional UART Transceiver

### 4.1 Introduction

The UART transceiver module serves as the top-level module that integrates the transmitter and receiver into a complete UART communication interface. This hierarchical design approach allows modularity, code reusability, and simplified testing. The module instantiates both transmitter and receiver sub-modules with matching parameter passing.

Signal routing within the transceiver creates independent transmit and receive data paths while sharing clock and reset common control signals. The design maintains separate data buses (`data_bits_tx` and `data_bits_rx`) to implement bidirectional communication without interference. Control signals handle `send_valid`, `tx_ready`, and `rx_valid` to coordinate data flow and indicate system status.

The transceiver supports full-duplex operation, allowing simultaneous transmission and reception operations for bidirectional communication protocols. This design approach enables easy modification of individual transmission or reception characteristics due to its modularity and parametric implementation.

## 4.2 RTL Code in System Verilog

```

`timescale 1ns / 1ps
module uart #(
    parameter
        WORD_SIZE = 8, // 8 bits per word
        PULSE_WIDTH = 4, // PULSE_WIDTH = CLOCK_FREQ/BAUD, CLOCK_FREQ = 100000000, BAUD = 115200, CLK_PERIOD = 10
        PACKET_SIZE = 10 // start, word, stop
    )
input logic clk, rstn,
            send_valid,
            rx,
input logic [WORD_SIZE-1:0] data_bits_tx,
output logic [WORD_SIZE-1:0] data_bits_rx,
output logic rx_valid,
            tx_ready, tx
);

// instantiate the transmitter
transmitter #(
    .WORD_SIZE(WORD_SIZE),
    .PULSE_WIDTH(PULSE_WIDTH),
    .PACKET_SIZE(PACKET_SIZE)
) UART_TX (
    .clk(clk),
    .rstn(rstn),
    .send_valid(send_valid),
    .data_bits(data_bits_tx),
    .tx_ready(tx_ready),
    .tx(tx)
);

// instantiate the receiver
reciever #(
    .WORD_SIZE(WORD_SIZE),
    .PULSE_WIDTH(PULSE_WIDTH),
    .PACKET_SIZE(PACKET_SIZE)
) UART_RX (
    .clk(clk),
    .rstn(rstn),
    .data_bits(data_bits_rx),
    .rx(rx),
    .rx_valid(rx_valid)
);
endmodule

```

Figure 11: RTL design of UART transceiver module

## 4.3 RTL design view

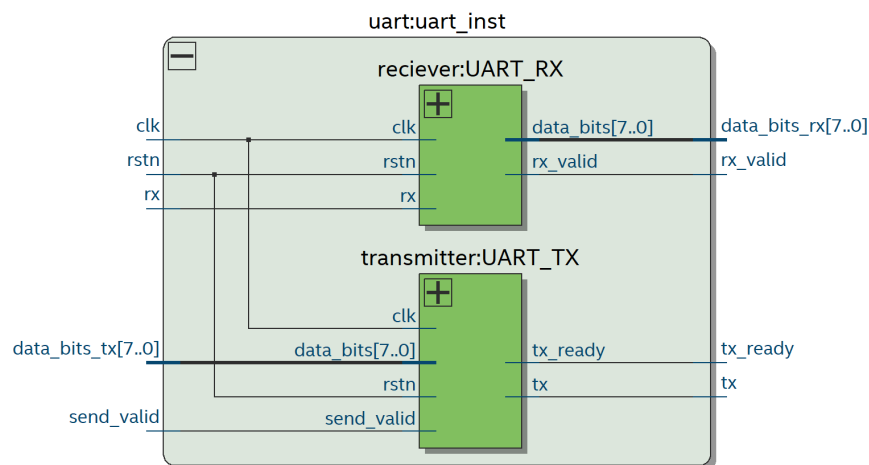


Figure 12: UART transceiver module block diagram



## 4.4 Verification Test Bench in System Verilog

```

timescale 1ns / 1ps

module uart_tb;
// parameters
localparam WORD_SIZE = 8,           // 8 bits per word
            PULSE_WIDTH = 4,        // PULSE_WIDTH = CLOCK_FREQ/BAUD, CLOCK_FREQ = 100000000, BAUD = 115200, CLK_PERIOD = 10
            PACKET_SIZE = 10,       // start, word, stop
            CLK_PERIOD = 10;        // 100MHz

// signals in test bench
logic clk = 0;
logic rstn = 0; // start in reset mode
logic send_valid = 0;
logic tx_ready;
logic tx;
logic rx = 1;
logic rx_valid;

logic [WORD_SIZE-1:0] data_bits_tx; // data to transmit
logic [WORD_SIZE-1:0] data_bits_rx; // data recieved
logic [WORD_SIZE-1:0] test_values [0:9]; // words for 10 test cases

// clock generation
always # (CLK_PERIOD/2) clk <= !clk; // 10 ns period

// instantiate UART module
uart #(
    .WORD_SIZE(WORD_SIZE),
    .PULSE_WIDTH(PULSE_WIDTH),
    .PACKET_SIZE(PACKET_SIZE)
) dut (
    .clk(clk),
    .rstn(rstn),
    .send_valid(send_valid),
    .rx(rx),
    .data_bits_tx(data_bits_tx),
    .data_bits_rx(data_bits_rx),
    .rx_valid(rx_valid),
    .tx_ready(tx_ready),
    .tx(tx)
);

// generate test cases
initial begin
    test_values[0] = 8'h55;
    test_values[1] = 8'hA3;
    test_values[2] = 8'h7E;
    test_values[3] = 8'h00;
    test_values[4] = 8'hFF;
    test_values[5] = 8'hC3;
    test_values[6] = 8'h3C;
    test_values[7] = 8'h5A;
    test_values[8] = 8'h81;
    test_values[9] = 8'h1E;
end

// connecting tx and rx.
always @(posedge clk) begin
    #1 rx = tx;
end

// test sequence
initial begin
    $dumpfile ("dump.vcd"); $dumpvars;

    // reset
    #20 rstn = 1; // remove reset after 20 ns (2 clks)
    repeat(5) @(posedge clk) #1;

    // test case - sending single word
    wait (tx_ready); // wait till tx is ready. ready in IDLE
    data_bits_tx = 8'b00100001; // start sending
    @(posedge clk) #1 send_valid = 1; // send signal pulse ends
    @(posedge clk) #1 send_valid = 0; // send signal pulse ends
    #10 $display("sending %b", data_bits_tx); // display the sending message (debugging)

    @(posedge rx_valid); // wait until rx is valid
    @(posedge clk); // wait for data to be fully latched
    #1 $display("Received: %b", data_bits_rx); // display the recieved message (debugging)

    // send test cases (10 words)
    for (int i = 0; i < 10; i = i+1) begin
        //repeat (10) begin
            repeat (5) @(posedge clk); // add a delay
            // repeat ($random_range(1,20)) @(posedge clk); // random delay. worked in vivado. not supported in quartus.
            wait (tx_ready); // wait till tx is ready. ready in IDLE
            data_bits_tx = test_values[i];
            // data_bits_tx = $random(); // test pattern [7:0] recieve is 0,01001001,1. random test cases. worked in vivado. not supported in quar

            @(posedge clk) #1 send_valid = 1; // start sending
            @(posedge clk) #1 send_valid = 0; // send signal pulse ends
            #10 $display("sending %b", data_bits_tx); // display the sending message (debugging)


            @(posedge rx_valid); // wait until rx is valid
            @(posedge clk); // wait for data to be fully latched
            #1 $display("Received: %b", data_bits_rx); // display the recieved message (debugging)
        end
    end // test sequence

    // count uart bits - for waveform
    int bits;
    initial forever begin
        bits = 0;
        wait (!tx);
        for (int j = 0; j < PACKET_SIZE; j = j+1) begin
            bits += 1;
            repeat (PULSE_WIDTH) @(posedge clk);
        end
    end
endmodule


```

Figure 13: Test bench code of UART transceiver module

## 4.5 Test bench simulation

 

 (a) Capture of all transmissions (Modelsim Altera)



(b) Zoomed in transmission of one word (Modelsim Altera)

```
# sending 00100001
# Received: 00100001
# sending 01010101
# Received: 01010101
# sending 10100011
# Received: 10100011
# sending 01111110
# Received: 01111110
# sending 00000000
# Received: 00000000
# sending 11111111
# Received: 11111111
# sending 11000011
# Received: 11000011
# sending 00111100
# Received: 00111100
# sending 01011010
# Received: 01011010
# sending 10000001
# Received: 10000001
# sending 00011110
# Received: 00011110
```

(c) UART test bench console output of transmitting and receiving data

Figure 14: UART test bench simulation timing diagram waveforms

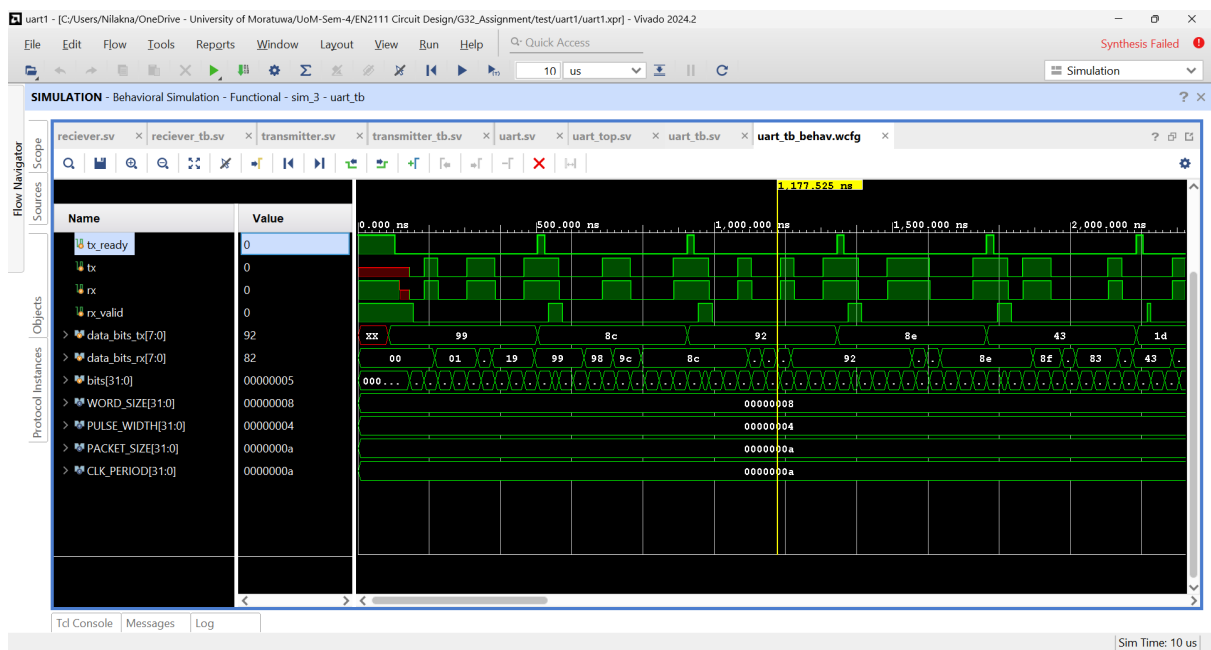


Figure 15: Vivado Simulation

## 5 Implementation on DEO Nano FPGA

### 5.1 Introduction

The UART top module represents the system-level implementation designed for FPGA deployment, incorporating practical considerations for real-world hardware interfaces. The module instantiates the complete UART transceiver with parameters configured for 115200 baud operation on a 50MHz system clock for DEO Nano, requiring a pulse width of 434 clock cycles per bit period. This configuration demonstrates proper timing calculation for reliable serial communication.

The implementation includes a continuous transmission system that automatically re-transmits a fixed data pattern (`data_bits_rx`) whenever the transmitter becomes ready, creating a predictable test pattern for system verification and debugging. The `send_valid` signal ensures proper timing and prevents glitched false transmissions. Reset signal is held high for this testing implementation.

Data visualization and monitoring are implemented through LED output mapping, where received data is latched (to `data_latch`) and displayed on the FPGA's LED array. The latching mechanism ensures that the received data remains visible between transmission events, providing immediate visual feedback for verification. The clock domain considerations are addressed through synchronous design, ensuring reliable operation throughout the system. The pin assignment uses dedicated GPIO pins for UART signals. This top-level integration ensures proper I/O assignment, parameter calculation, and system-level verification approaches.

## 5.2 Pin plan

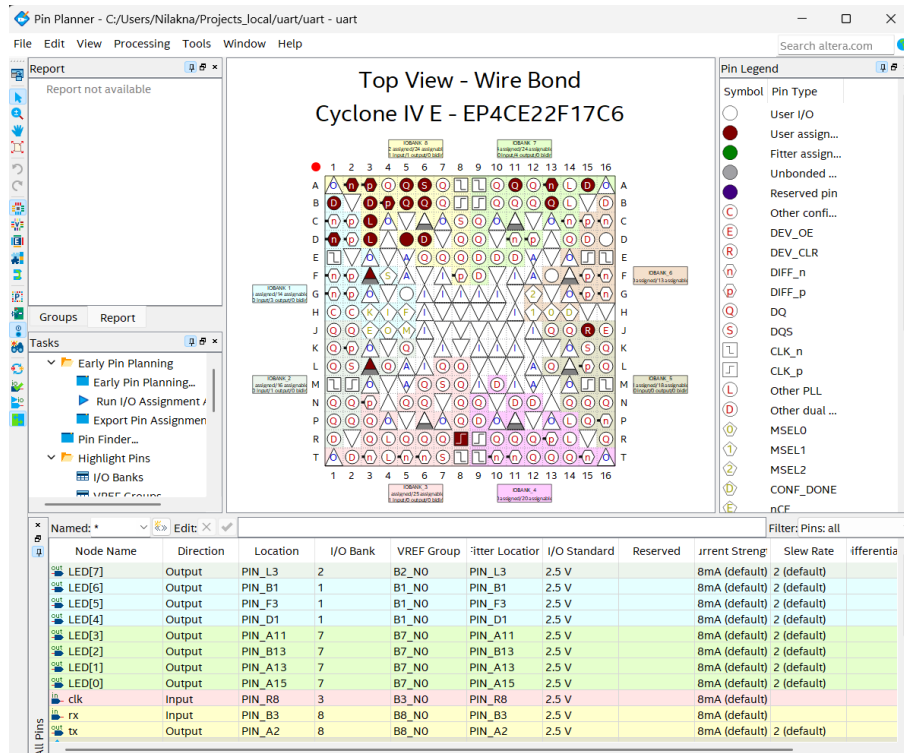


Figure 16: Pin planner for DEO Nano Board

Pins should be assigned to clk, tx, rx, and LED in the top module. Referring to the user manual [1] clock is assigned to 50 MHz oscillator via PIN\_R8. The input rx is assigned to PIN\_B3, pin 7 of GPIO-0 header named GPIO\_02, while the output tx is assigned to PIN\_A2, pin 5 of GPIO-0 header named GPIO\_04 (refer to 3.5 expansion headers [1]). The LED signals are connected to the onboard LEDs as mentioned in Table 3-2 of the user manual [1].

## 5.3 RTL Code of the top module

```
// testing code for the uart module

module uart_top (
    input logic clk,           // 50MHz clock from DE0-Nano
    output logic tx,           // pin 5 of JP1
    input logic rx,            // pin 7 of JP1
    output logic [7:0] LED     // LED7 to LED0
);

    logic [7:0] data_bits_tx = 8'b00000110; // tx data
    logic [7:0] data_bits_rx;
    logic rx_valid;
    logic tx_ready;
    logic send_valid;
    logic rstn;

    assign rstn = 1'b1;

    uart #(
        .WORD_SIZE(8),
        .PULSE_WIDTH(434),
        .PACKET_SIZE(10)
    ) uart_inst (
        .clk(clk),
        .rstn(rstn),
        .send_valid(send_valid),
        .data_bits_tx(data_bits_tx),
        .data_bits_rx(data_bits_rx),
        .rx_valid(rx_valid),
        .tx_ready(tx_ready),
        .tx(tx),
        .rx(rx)
    );

    logic [7:0] data_latch;

    // send_valid signal
    always_ff @(posedge clk or negedge rstn) begin
        if (!rstn)
            send_valid <= 0;
        else if (tx_ready)
            send_valid <= 1;
        else
            send_valid <= 0;
    end

    // Latch data when rx_valid goes high
    always_ff @(posedge clk) begin
        if (!rstn)
            data_latch <= 8'b0;
        else if (rx_valid)
            data_latch <= data_bits_rx;
    end

    assign LED = data_latch;
endmodule
```

Figure 17: Top module RTL code for FPGA

## 5.4 RTL design view


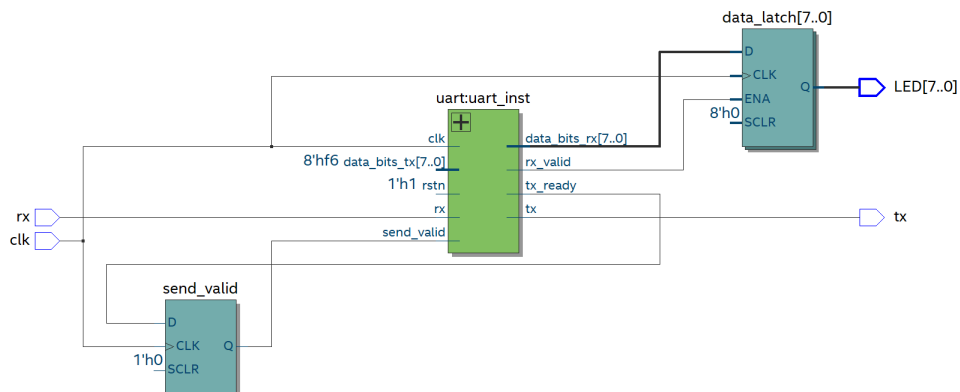


Figure 18: UART top module block diagram

## 5.5 Results on FPGA

 

(a) Payload 8'b00110110

(b) Payload 8'b11110110

Figure 19: Sample data sending from UART TX to RX

 


Figure 20: RX is '1' when transmitter sends no data



## References

- [1] Texas Instruments, *DEO Nano User's Guide*, Texas Instruments, May 2015, rev. A.  
[Online]. Available: <https://www.ti.com/lit/ug/tidu737/tidu737.pdf>